

Questions:

1. 5040, 7!
2. 68, 30, 4F, 18
3. Place the scope on the collector of the corresponding pnp transistor, trigger on falling edge
4. You would use high side drive, npn, and 1 to turn on, because the diode orientation is reversed
- 5.